

# Simplification of Logic Functions Using SOP, POS

## Lecture 4

Prepared by : Eng.Amani Safwat

# Introduction to Logic Simplification

Logic simplification is the process of reducing a complex logical expression to its simplest form without changing its output. The goals of simplification are:

- Reduce the number of gates and logic used in circuits.
- Save cost and power.
- Make the design easier to understand and maintain

# SOP

SOP (sum of product)


- Each term is a **product (AND) of variables or their complements**.
- Then all terms are summed together using OR.
- SOP is widely used because it is easy to convert into a logic circuit using **AND and OR gates**.

$$Y = A'B + AB'$$

- Each term like  $A'B$  is a product.
- All terms are summed using  $+$  (OR)

# SOP

$$Y = A'B + AB'$$

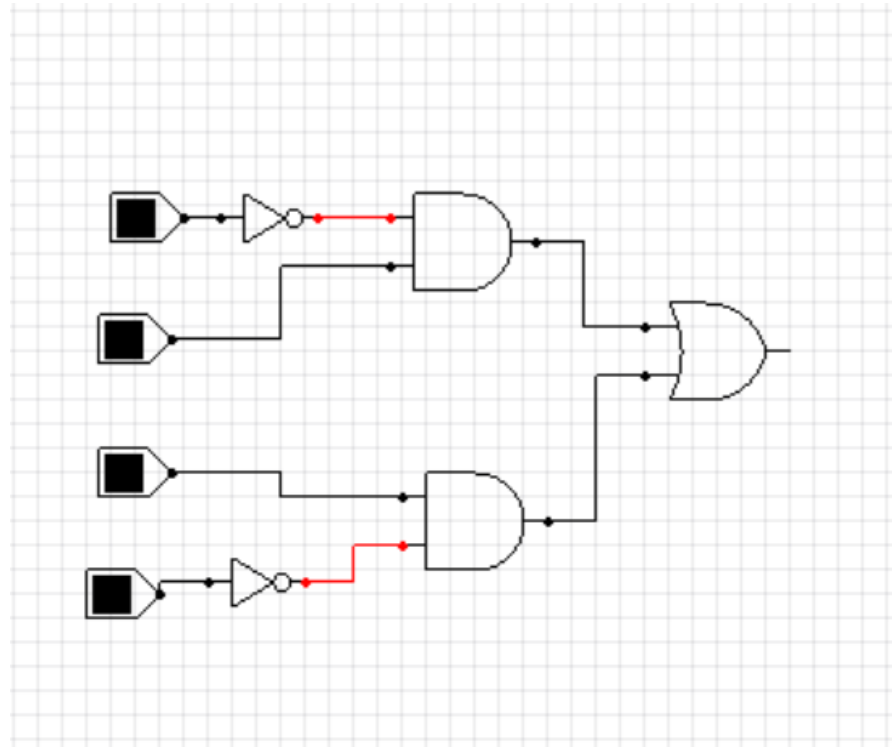


# POS

POS (product of sum)

- Each term is a **sum (OR) of variables or their complements**.
  - Then all terms are multiplied together using AND.
  - POS is sometimes used for designing circuits easily using **OR and AND gates**
- 
- $Y = (A + B')(A + B')$
  - Each term like  $(A + B')$  is a sum.
  - All terms are multiplied together (AND).

# POS

$$Y = (A' + B) \cdot (A + B')$$

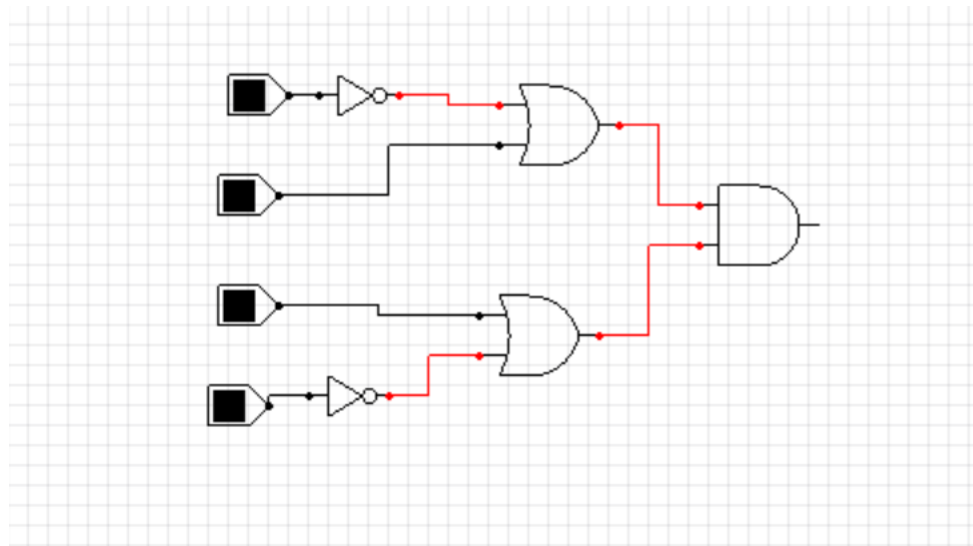

# Canonical SOP

$$F_{(A,B)} = \sum (1,3)$$

Canonical SOP is the **sum of all minterms that give output 1.**

Each minterm is the **AND of all variables, complemented or not.**

Called canonical because it represents the function exactly, without simplification

the function  $Y = (A, B)$  is equal to:

$$(A, B) = (0, 1), (1, 0)$$

The standard SOP formula is:

$$Y = A'B + AB'$$

# Canonical POS

$$F_{(A,B)} = \prod (0,2)$$

Canonical POS is the **product of all maxterms that give output 0.**

Each maxterm is the **OR of all variables, complemented or not, depending on value.**

Called canonical because it represents the function exactly before any simplification

the function  $Y = (A, B)$  is equal to:

$$(A, B) = (1, 1), (1, 0)$$

The standard POS formula is:

$$Y = (A' + B).(A' + B)$$



# Example

From this table find:

1.SOP

2.POS

3.Canonical SOP

4. Canonical POS

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

# Example

To find SOP :

We look at the number of one in the result, write the number of variables, and then add negation to the input whose value is zero.

$$F = A'B'C + A'BC + AB'C' + ABC'$$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

# Example

To find POS :

We look at the zero in the result, write down the number of variables, and then add the negative to the input whose value is one.

$$F = (A+B+C).(A+B'+C).(A'+B+C').(A'+B'+C')$$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

# Example

Canonical SOP:

0 0 1   0 1 1   1 0 0   1 1 0  
          1           3           4           6

$$F_{(A,B,C)} = \Sigma(1,3,4,6)$$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

# Example

Canonical POS

0 0 0   0 1 0   1 0 1   1 1 1

0            2            5            7

$$F_{(A,B,C)} = \Pi(0,2,5,7)$$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0