

Physics Course

Aden German International University

Aden – Yemen



**What is
a Charge ?**



What is a Charge ?



- Charge is the inherent property of matter that feels force of attraction out repulsion due to excess or deficiency of electrons.
- It is of 2 types :
 - A. Positive Charge (Due to electron deficiency)
 - B. Negative Charge (Due to excess of electrons)
- Its S.I. unit is Coulombs denoted by 'C'.
- It is detected and measured using a device called Electroscope.



Properties Of Charge



Properties of Charge



- The total charge of the universe is conserved i.e. constant
- Unlike Charges attract each other and like charges repel each other
- Charges are additive in nature
- Charges are always quantized i.e. $Q = n \times e$
where q = charge,
 n = no. of electrons
 e = charge on one electron i.e. $1.67 \times 10^{-19} \text{ C}$
- Charge is relativistically constant



**What is
Electricity ?**





What is Electricity ?



- Electricity is a form of a energy that can be easily changed to many other forms.
- It can also be defined as flow of electrons in a circuit.





Electric Current




Electric Current



- It is the rate of flow of electric charge (or electrons) through a conductor i.e.

$$I = Q/t = ne/t \quad \text{where } I \text{ stands for current}$$

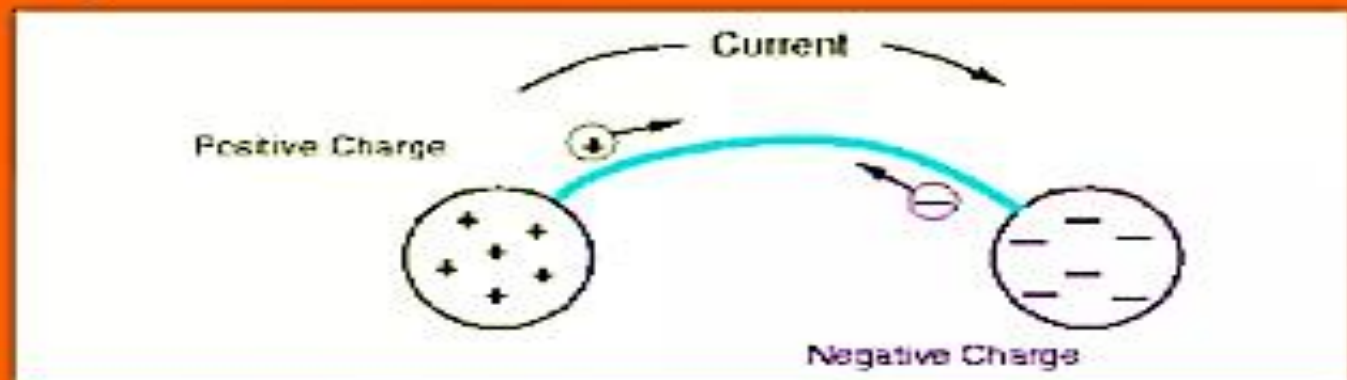- It is a scalar quantity
- Its S.I. unit is coulomb per second or amperes (A)
- It is measured by a device called Ammeter
- Its direction is taken opposite to the flow of electrons
- It flows as a result of potential difference across the ends of a conductor





Electric Field



Electric Field



- It is the 3 dimensional space around a charge in which the force of attraction or repulsion can be felt.

➤ Electric Field Intensity

- ❖ It is the force experienced by a unit positive test charge at a given point in an electric field.
- It is denoted by 'E'
- Its S.I. unit is newton per coulomb (N/C)
- It is a vector quantity




Electric Potential and Potential Difference

Electric Potential



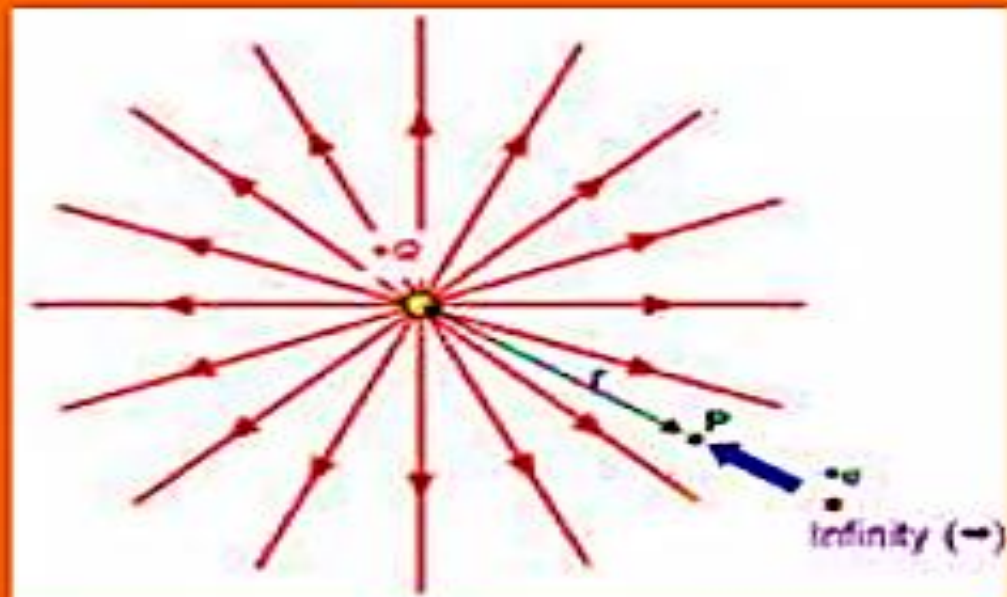- It is the amount of work done in bringing a unit positive charge from infinity to a given point in the electric field.
- It is a scalar quantity
- Its S.I. unit is joules per coulomb or volts (V)





Potential Difference



- It is the amount of work done in bringing a unit positive charge from one point to another point in an electric field.
- It is a scalar quantity
- Its S.I. unit is joules per coulomb or volts (V)
- It is responsible for the flow of current in a conductor.
- Measured by a device called Voltmeter.





Ohm's Law





Ohm's Law



GEORG SIMON OHM
1789-1854

- It was stated by Georg Simon Ohm
- It states that at constant physical conditions like temperature are kept constant then the amount of current flowing through a conductor is directly proportional to the potential difference across its ends i.e.

$$I \propto V$$

$V = IR$ where R is constant called Resistance


- According to this law conductors are divide into -
 1. Ohmic conductors (follow ohm's law)
 2. Non- ohmic conductors (do not follow ohm's law)




I-V Graphs for Conductors



ohmic

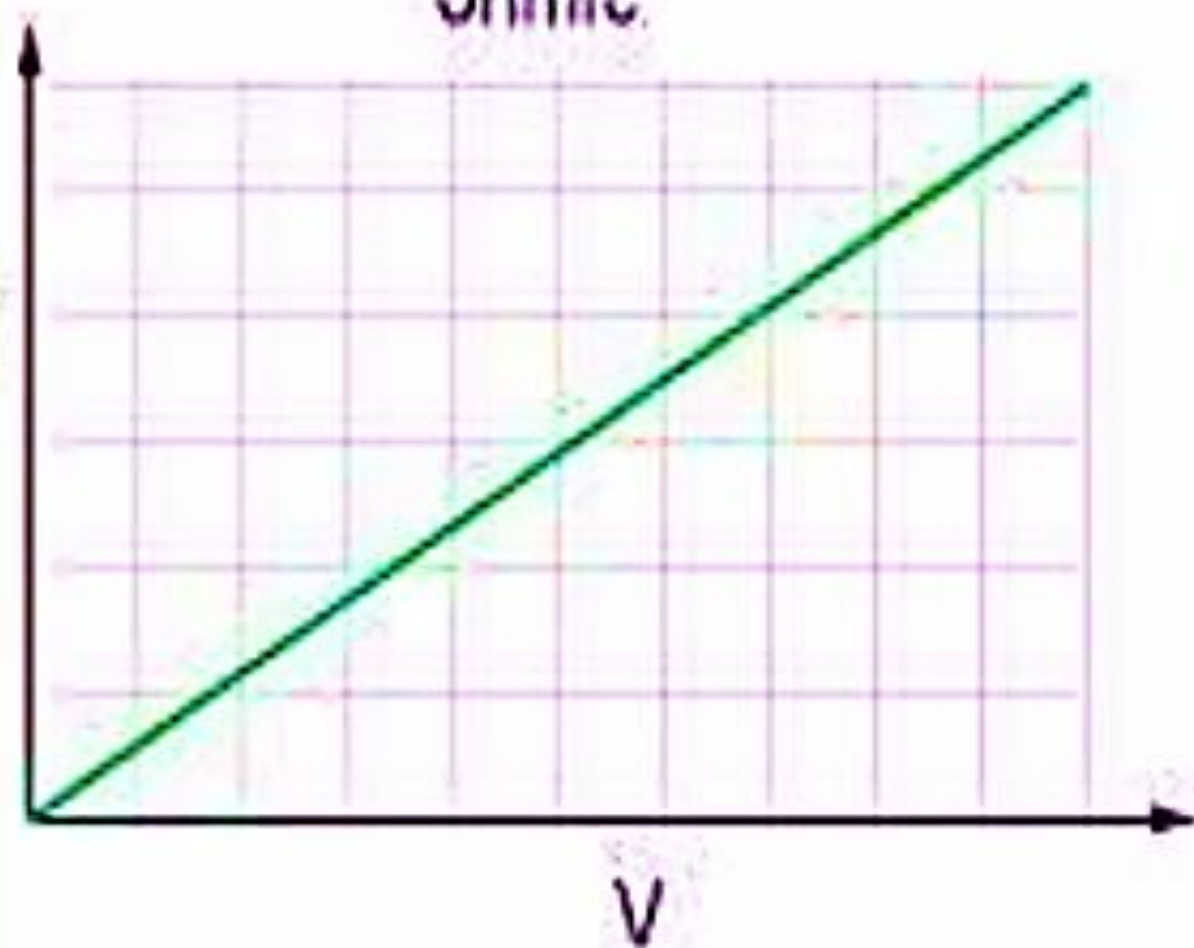

non-ohmic

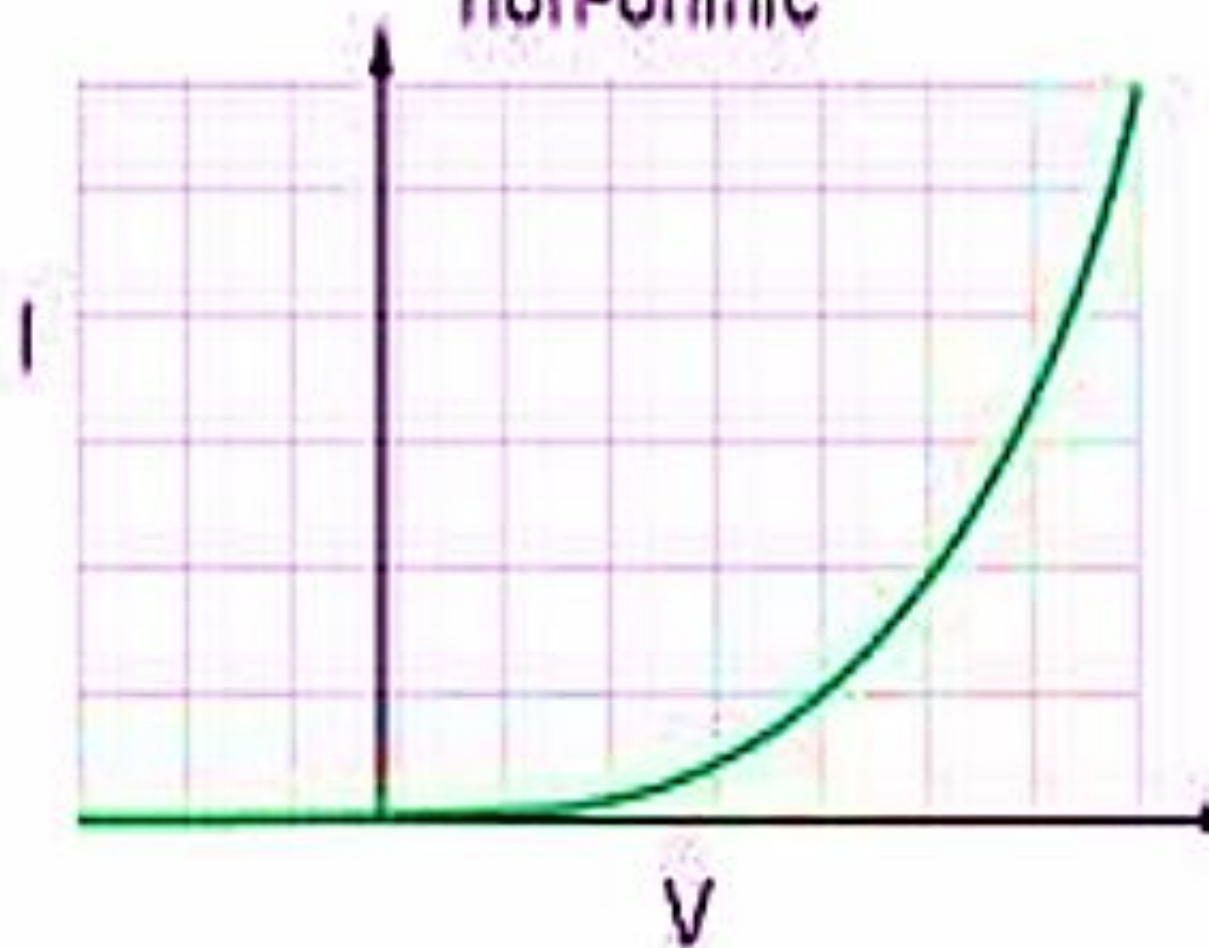




Resistance and Resistivity

Resistance



- It is defined as the hindrance to the flow of current
- It is the ratio of potential difference to current i.e.
 $R = V/I$
- Its S.I. unit is volts per ampere or Ohm (denoted by Ω)
- Reciprocal of resistance is called Conductance (C) .
S.I. unit Ohm^{-1} i.e. Ω^{-1}

high resistance
low current

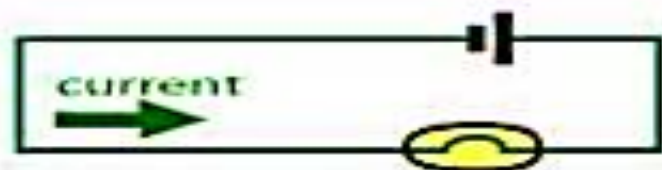

low resistance
high current






Factors affecting Resistance



- $R \propto \text{Length (l)} \dots\dots\dots\text{(i)}$
- $R \propto 1/\text{Area of cross section of conductor (A)} \dots\dots\dots\text{(ii)}$
- $R \propto \text{Resistivity (}\rho\text{)} \dots\dots\dots\text{(iii)}$

From (i), (ii) and (iii) we get

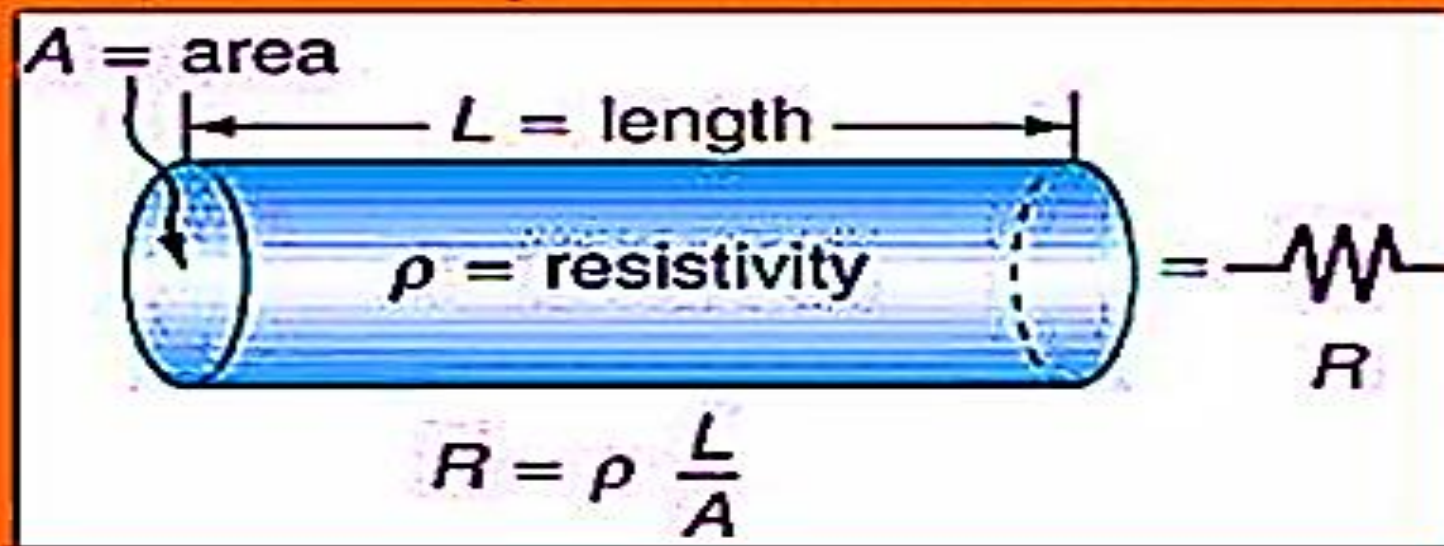➤ $R = \rho l/A$ where constant “ ρ ” is the specific resistance of the conductor





Types of Resistances



- **Fixed Resistances:** Their value does not change under constant physical conditions. They are set at a particular value
- **Variable Resistances:** Their resistance can be easily changed by changing area of cross section and length



Fixed Resistors



Variable resistance or Rheostat




Electric Circuit and Its Components



Electric Circuit



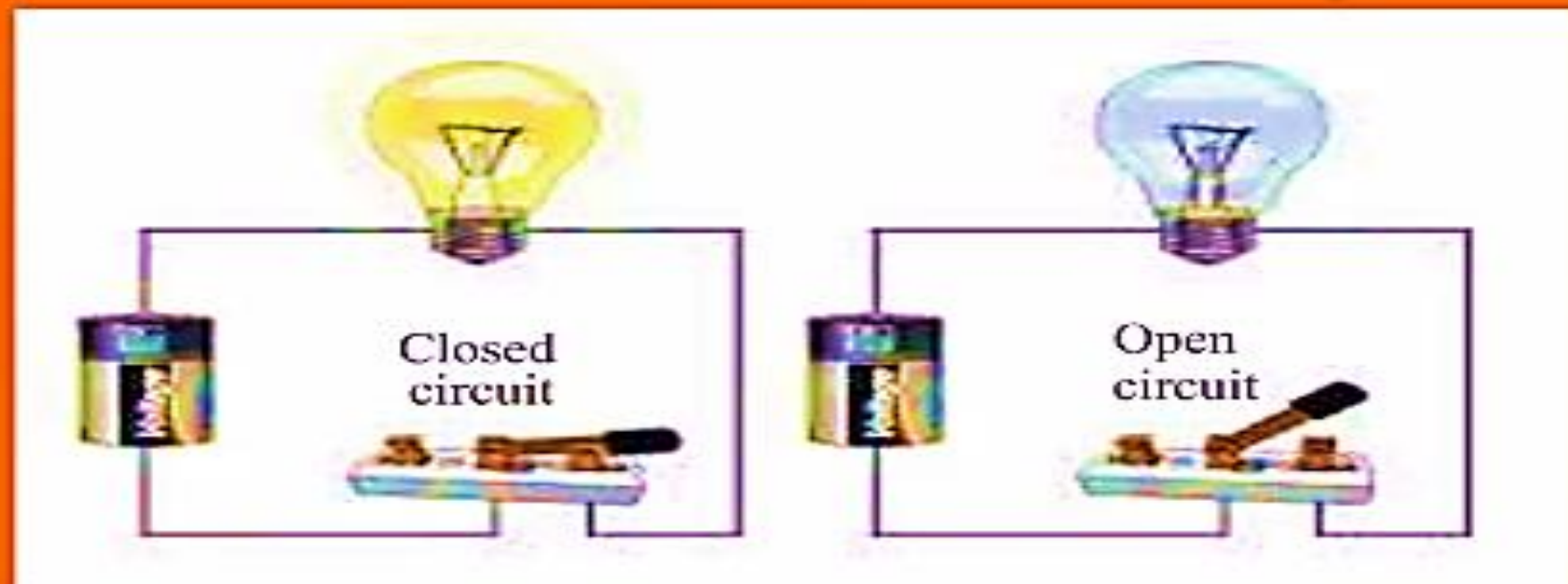- A closed path in which electric current can flow is called an electric circuit
- There are 2 types of circuits –
 1. Open Circuit: No current flows
 2. Closed Circuit: Current flows continuously



Electric Circuit Symbols



1	An electric cell	
2	A battery or a combination of cells	
3	Plug key or switch (open)	
4	Plug key or switch (closed)	
5	A wire joint	
6	Wires crossing without joining	
7	Electric bulb	
8	A resistor of resistance R	
9	Variable resistance or rheostat	
10	Ammeter	
11	Voltmeter	




Measuring Devices



Ammeter




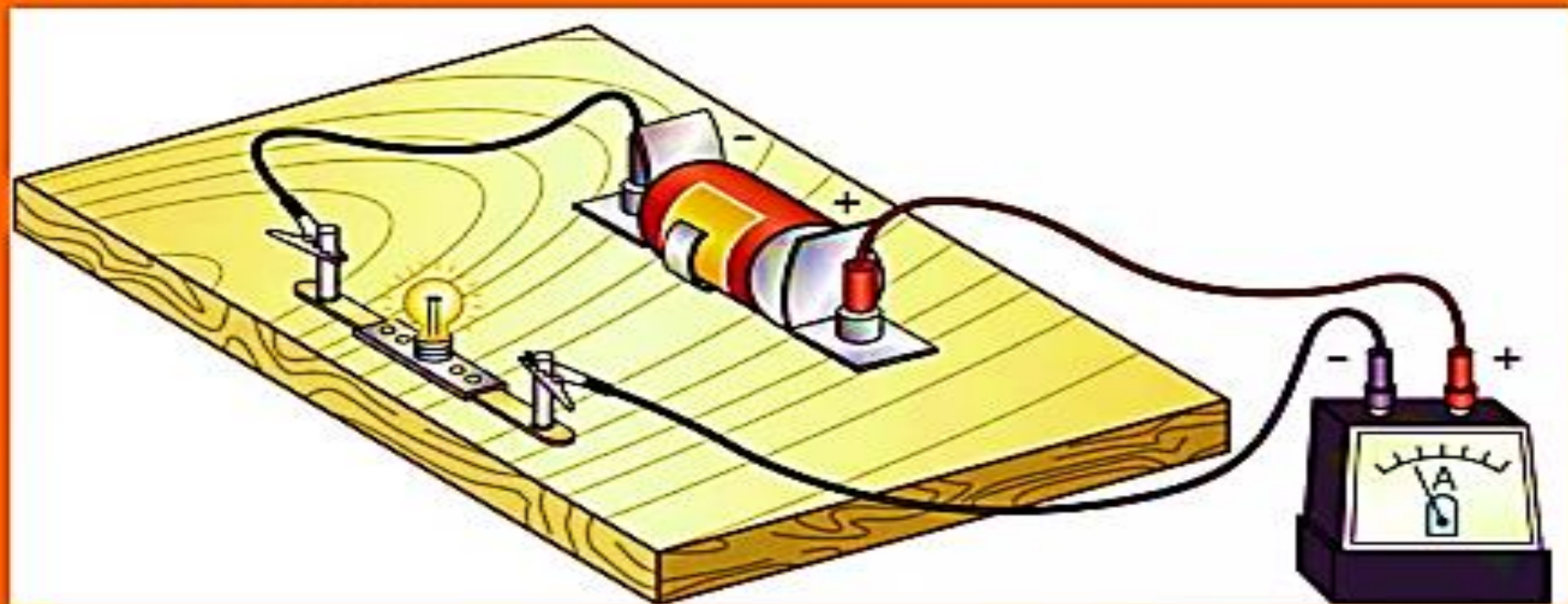
- It must be connected in series in the circuit.
- Positive side of ammeter must be connected nearest to the positive terminal of the battery (electric cell), and vice versa.





Voltmeter

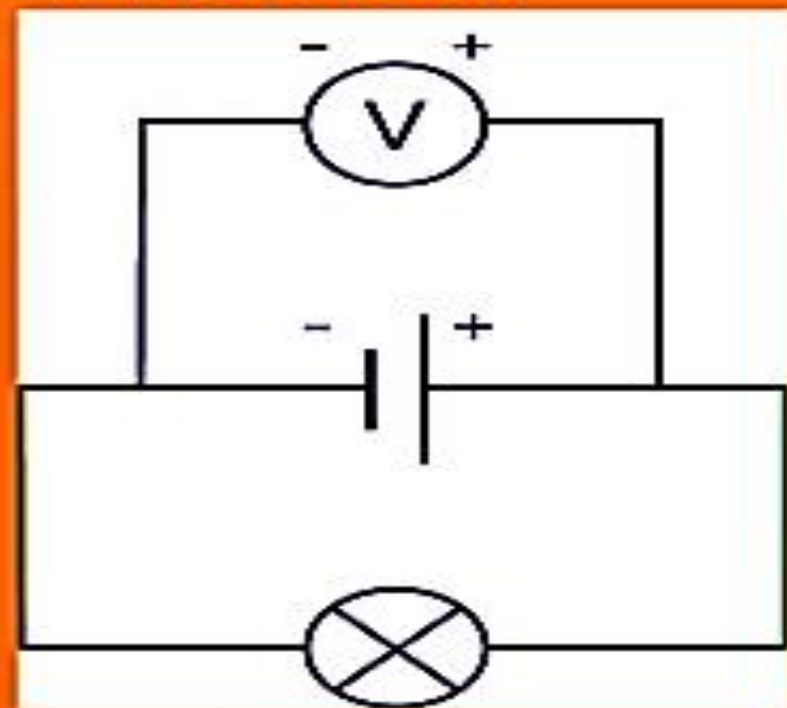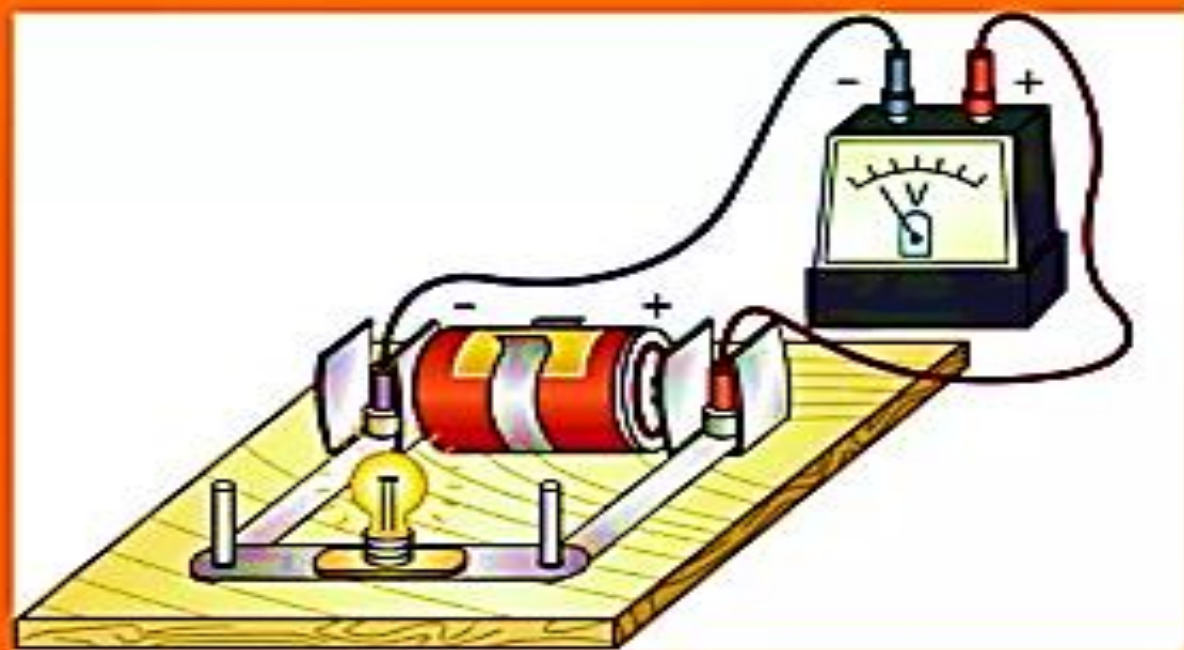- Voltmeters must be connected in parallel to the circuit.
- The positive side of voltmeter is connected to the positive terminal of the cell, and vice versa.





Combination of Resistances



Combination of Resistances



There are 2 ways of joining resistors together

- 1. Series Combination**
- 2. Parallel Combination**



Resistance in Series



- The figure shows three resistances R_1, R_2, R_3 connected in series. Now suppose potential difference across resistance R_1 is V_1 , R_2 is V_2 and R_3 is V_3 . Let potential difference across battery be V , then :

$$V = V_1 + V_2 + V_3.$$

Applying Ohm's law to the whole circuit : $V = IR$(1)

Applying Ohm's law to the three resistors separately, we get:

$$V_1 = I \times R_1. (2)$$

$$V_2 = I \times R_2. (3)$$

$$V_3 = I \times R_3. (4)$$


Substituting (2), (3), (4) in (1)

$$IR = IR_1 + IR_2 + IR_3$$

$$\text{OR, } IR = I(R_1 + R_2 + R_3)$$

$$\text{Or, } R = R_1 + R_2 + R_3.$$

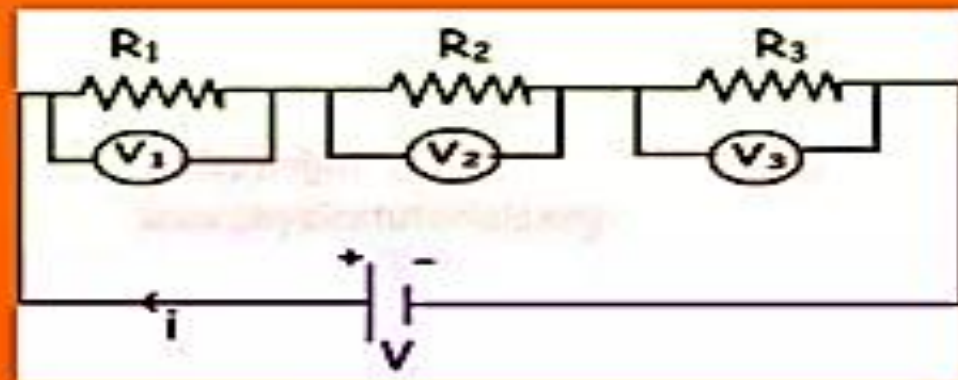Therefore we conclude that the sum total resistance in a series resistance connection is equal to the sum of all the resistances.





Resistance in Parallel



- The figure shows three resistances R_1, R_2, R_3 connected in series. Now suppose current across resistance R_1 is I_1 , R_2 is I_2 and R_3 is I_3 . Let total current in the circuit be I , then:

$$I = I_1 + I_2 + I_3.$$

Applying Ohm's law to the whole circuit : $I = V/R$(1)

Applying Ohm's law to the three resistors separately, we get:

$$I_1 = V / R_1. (2)$$

$$I_2 = V / R_2. (3)$$

$$I_3 = V / R_3. (4)$$


Substituting (2), (3), (4) in (1)

$$V/R = V/R_1 + V/R_2 + V/R_3$$

$$\text{OR, } V/R = V (1/R_1 + 1/R_2 + 1/R_3)$$

$$\text{Or, } 1/R = 1/R_1 + 1/R_2 + 1/R_3 .$$

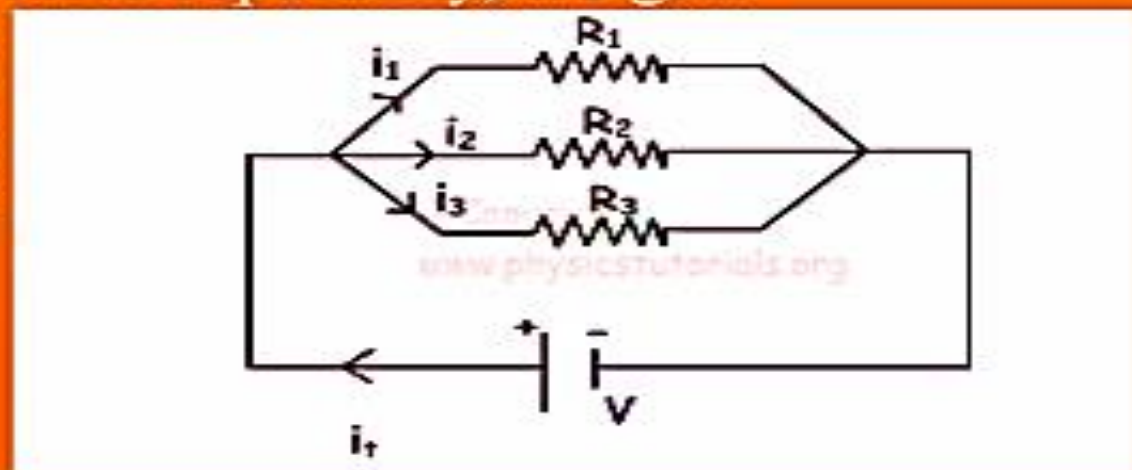Therefore we conclude that the sum total resistance in a parallel resistance connection is equal to the sum of reciprocal of all the resistances.



THANK YOU

THANK YOU