

# Lecture 3



## LOGIC GATES

prepared by Eng.shada Abduladeem

# Variable and Functions
  
## Logic Expression






- We can describe the system as a logic expression
  - Input: switch control  $x$
  - Output: light bulb  $L$
- Light  $L$  is a function of the input variable  $x$ 
  - $L = 1$  if  $x = 1$
  - $L = 0$  if  $x = 0$
- **Thus,  $L(x) = x$**



# Variable and Functions
     
## Two Switch Application-Series Connection

- What if we use two switches to control the light?
  - $x_1, x_2$  are control **inputs** to the switches
  - We first connect switches in series
- When will the light be on?



- Logical expression to describe behaviour
  - $L(x_1, x_2) = x_1 \cdot x_2$

## The AND Gate

---



- **This is an AND gate.**
- **So, if the two inputs signals are asserted (high) the output will also be asserted. Otherwise, the output will be deasserted (low).**






Truth Table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

# Variable and Functions
     
## Two Switch Application-Parallel Connection

- We again use two switches to control the light
  - $x_1, x_2$  are control inputs to the switches
  - Connect switches in parallel
- When will the light be on?



- Logical expression to describe behaviour
  - $L(x_1, x_2) = x_1 + x_2$

## The OR Gate

---




- › **This is an OR gate.**
- › **So, if either of the two input signals are asserted, or both of them are, the output will be asserted.**

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

# Inversion
 
## NOT Operation Notation

- Different names for NOT operation
  - Complement, Invert, Inverse
- Different notations for NOT operation
  - $\overline{x} = x' = !x = \sim x$



Symbol


Truth Table

A	Y
0	1
1	0

Input

Output

# Input output signals for gates

 






# Variable and Functions
 
## Three Switch Application

- AND and OR functions
  - Building blocks for larger circuits
- Example with three switches
  - $x_1$ ,  $x_2$ , and  $x_3$  are control inputs to the switches
  - Series-parallel connection
- When will the light be on?




  

# Logic Gates and Networks
 
## Digital System Designer Concern

- Digital system designer faced with two basic issues
  - Determine function of an existing logic network → **Analysis**
  - Designing a logic network to implement the desired function → **Synthesis**




STEP 1 :  
ANALYSING  
LOGIC CIRCUITS

# Logic Gates and Networks
 
## Analysis of Logic Network

- Convert logic network into logic expression



$f =$

$$f = a + b$$


$$f = x_1' + b$$

$$f = x_1' + (x_1 \cdot x_2)$$

# Logic Gates and Networks
 
## Analysis of Logic Network

- Convert logic network into logic expression



$$f =$$

$$f = a'$$


$$f = (x_1 + b)'$$

$$f = (x_1 + (x_1 \cdot x_2))'$$

# Logic Gates and Networks
 
## Analysis of Logic Network

- Convert logic network into logic expression



f =

$$f = t1 + t2$$

$$f = (a \cdot b)' + t2$$

$$f = (a \cdot b)' + (c \cdot d)'$$

TO TEST CIRCUIT FUNCTIONALITY

# **1. TRUTH TABLE**



# Truth Table

## Introduction

**Left Side:**  
All possible  
combinations for  
input values

No of combinations =  $2^n$   
where  $n$  = No of inputs

x1	x2		$x1 \cdot x2$	$x1 + x2$
0	0		0	0
0	1		0	1
1	0		0	1
1	1		1	1

**Right Side:**  
Values for outputs

**Truth table for  
AND Operation**

**Truth table for OR  
Operation**

# Truth Table

## Introduction

- Advantages
  - Only one truth table
  - Intuitive to read
- Disadvantages
  - Size explosion

a	b	F
0	0	0
0	1	0
1	0	1
1	1	1

2-input truth table

a	b	c	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

3-input truth table

a	b	c	d	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

4-input truth table

How many lines are needed if you have 8 inputs?





5-input truth table?

# Logic Gates and Networks

  
## Analysis of Logic Network

- Another way to specify circuit functionality – truth table
  - Consider what happens to output  $f$  for all possible inputs







$x_1$	$x_2$	$F$
0	0	1
0	1	1
1	0	0
1	1	1

## Example 2 :

 

$$g = x1' + x2$$


x1	x2	G
0	0	1
0	1	1
1	0	0
1	1	1

    

# Logic Gates and Networks

 
## Functional Equivalence

- You may have noticed we got the same truth table for both examples
  - Logic circuits are functionally equivalent
- Logic function can be implemented in a variety of ways
  - Designer wants to use the simpler one – lower cost
  - How do we determine the best implementation?
    - Manipulate function using a set of rules (Boolean Algebra)
    - Other techniques discussed in Chapter 4



$$f = x1' + (x1 \cdot x2)$$

x1	x2	F
0	0	1
0	1	1
1	0	0
1	1	1

 

$$g = x1' + x2$$


x1	x2	G
0	0	1
0	1	1
1	0	0
1	1	1

2. Timing diagram.


# Logic Gates and Networks
 
## Timing Diagram

- Yet another way to describe logic circuit behaviour – timing diagram
  - Time runs from left to right
  - Each input value is held for a fixed period
  - Waveform shown indicating **inputs, output, and internal signal** values




x1	x2	F
0	0	1
0	1	1
1	0	0
1	1	1

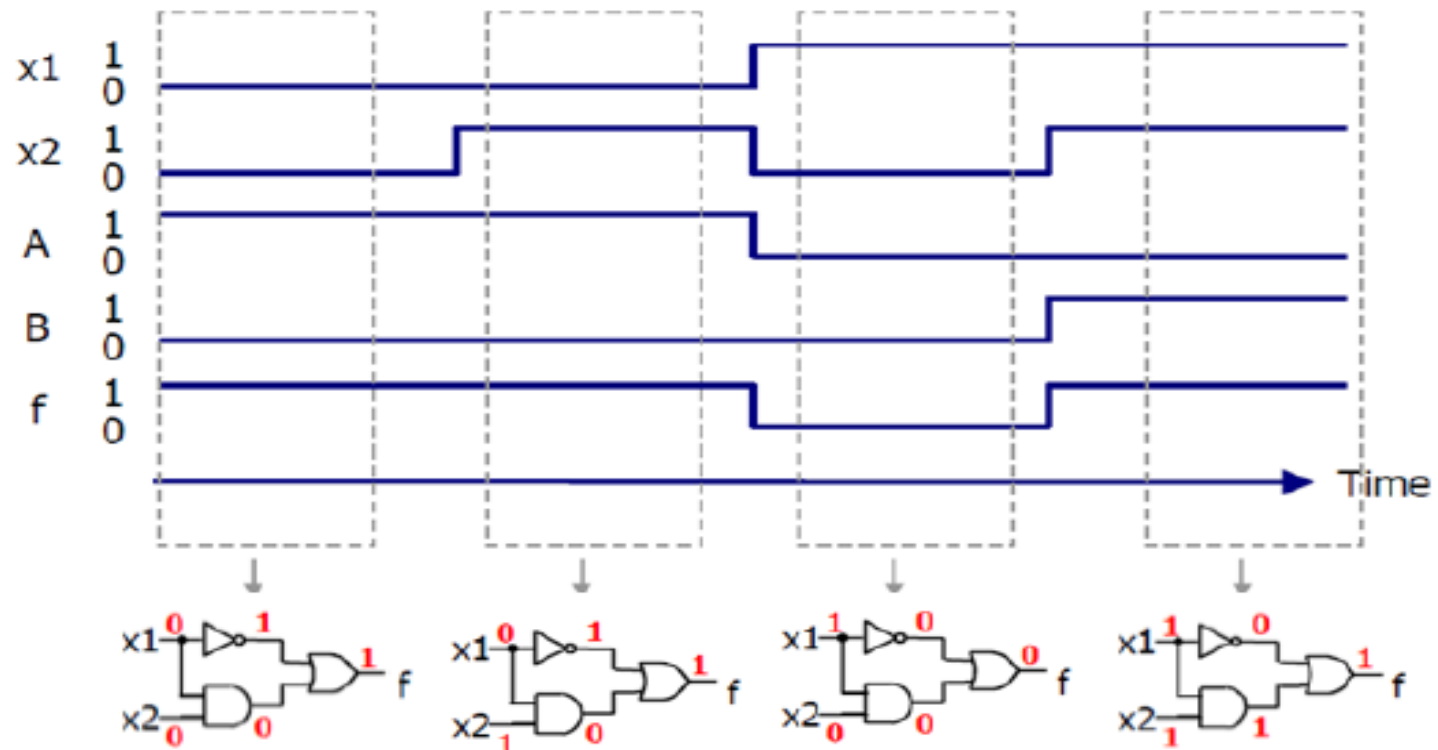

# Logic Gates and Networks
 
## Synthesis of Logic Network

- Second design issue – **Synthesis**
  - How do I go from a logic expression to a logic circuit?








# Logic Gates and Networks
   
## Synthesis of Logic Network

- Convert  $f = x1' + (x1 \cdot x2)$  to a logic circuit
  - What are your **inputs**?
    - $x1, x2$
  - What are/is your **output(s)**?
    - $F$
  - How is the function evaluated?
    - Parentheses
    - NOT operation
    - OR operation




Symbol	Name	Description
( )	Parentheses	Evaluate expression nested in parentheses first
'	NOT	Evaluate from left to right
·	AND	Evaluate from left to right
+	OR	Evaluate from left to right


Convert  $H = a \cdot (b + c')'$  to a logic circuit

Convert  $R = (a \cdot b') \cdot (b + c')$  to a logic circuit

 - Convert  $H = a \cdot (b + c')$  to a logic circuit




 
- Convert  $R = (a \cdot b') \cdot (b + c')$  to a logic circuit





# Logic Gates and Networks
  
## Synthesis of Logic Network

- Convert  $F_{out} = (a \cdot b \cdot c)$  to a logic circuit
  - How do we implement a 3-input gate?
    - Using 2-input AND gates
    - Using 3-input AND gates



  
- Same for **OR** gates
- $J = k + l + m + n$



# Boolean Algebra
 
## ■ Everyday Boolean Logic:

- I will (i) go to lunch if Mohammed (m) goes OR Jawad (j) goes, AND Sami (s) does NOT go.
  - i -> will I go?
  - m -> Does Mohammed go?
  - j -> Does Jawad go?
  - s -> Does Sami go?



$$i = (m + j) \cdot (!s)$$

m	j	s	i
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

# Boolean Algebra : Single Variable Theorems

- We can derive single variable theorems (rules)
  - Assume  $x$  is a variable

**OR**

a	x	F
0	0	0
0	1	1
1	0	1
1	1	1

**AND**

a	x	F
0	0	0
0	1	0
1	0	0
1	1	1

**AND**

a	x	F
0	0	0
0	1	0
1	0	0
1	1	1

**AND**

a	x	F
0	0	0
0	1	0
1	0	0
1	1	1

5a.  $x \cdot 0 = 0$  (Null Elements)

5b.  $x + 1 = 1$

6a.  $x \cdot 1 = x$  (Identity)

6b.  $x + 0 = x$

7a.  $x \cdot x = x$  (Idempotent)

7b.  $x + x = x$

8a.  $x \cdot x' = 0$  (Complement)

8b.  $x + x' = 1$

9a.  $x'' = x$  (involution)

# Boolean Algebra : Duality

---

- Principle of duality

- Given a logic expression, its dual is obtained by replacing all “.” operators with “+” operators and all 0's with 1's
- The dual of any true statement is also true
- Axioms and theorem listed in pairs to illustrate duality

1a.  $0 \cdot 0 = 0$

1b.  $1 + 1 = 1$

2a.  $1 \cdot 1 = 1$

2b.  $0 + 0 = 0$

3a.  $0 \cdot 1 = 1 \cdot 0 = 0$

3b.  $0 + 1 = 1 + 0 = 1$

4a. If  $x = 0$ , then  $x' = 1$

4b. If  $x = 1$ , then  $x' = 0$

5a.  $x \cdot 0 = 0$

5b.  $x + 1 = 1$

6a.  $x \cdot 1 = x$

6b.  $x + 0 = x$

7a.  $x \cdot x = x$

7b.  $x + x = x$

8a.  $x \cdot x' = 0$

8b.  $x + x' = 1$

9.  $x'' = x$



## Boolean Algebra : Properties

---

- 2- and 3-variable identities – Properties

- x, y, and z are variables

10a.  $x \cdot y = y \cdot x$  *(Commutative)*

10b.  $x + y = y + x$

11a.  $x \cdot (y \cdot z) = (x \cdot y) \cdot z$  *(Associative)*

11b.  $x + (y + z) = (x + y) + z$

12a.  $x \cdot (y + z) = x \cdot y + x \cdot z$  *(Distributive)*

12b.  $x + (y \cdot z) = (x + y) \cdot (x + z)$  *this one is tricky!*

13a.  $x + x \cdot y = x$  *(Absorption)*

13b.  $x \cdot (x + y) = x$

14a.  $x \cdot y + x \cdot y' = x$  *(Combining)*

14b.  $(x + y) \cdot (x + y') = x$

15a.  $(x \cdot y)' = x' + y'$  *(DeMorgan's Theorem)*

15b.  $(x + y)' = x' \cdot y'$

16a.  $x + x' \cdot y = x + y$

16b.  $x \cdot (x' + y) = x \cdot y$

# Boolean Algebra: Properties

- How can we prove these properties?
  - Truth table
  - Algebraic Manipulation
- Show DeMorgan's Theorem works using a truth table
  - $(x \cdot y)' = x' + y'$



**LHS**



**RHS**

x	y	$(x \cdot y)$	$(x \cdot y)'$	$x'$	$y'$	$x' + y'$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

*Truth tables  
produce same  
result – functions  
are equivalent!*

## Boolean Algebra: Algebraic Manipulations Example

- Prove  $(x_1 + x_3) \cdot (x_1' + x_3') = x_1 \cdot x_3' + x_1' \cdot x_3$  using algebraic manipulation

$$\text{LHS} = (x_1 + x_3) \cdot (x_1' + x_3')$$

Use Distributive property 12a -  $x \cdot (y + z) = x \cdot y + x \cdot z$

$$\text{LHS} = (x_1 + x_3) \cdot x_1' + (x_1 + x_3) \cdot x_3'$$

Use Distributive property again

$$\text{LHS} = (x_1 \cdot x_1') + (x_3 \cdot x_1') + (x_1 \cdot x_3') + (x_3 \cdot x_3')$$

Use complement property 8a -  $x \cdot x' = 0$

$$\text{LHS} = 0 + (x_3 \cdot x_1') + (x_1 \cdot x_3') + 0$$

Use Identity 6b -  $x + 0 = x$

$$\text{LHS} = (x_3 \cdot x_1') + (x_1 \cdot x_3')$$

Use commutative property 10a -  $x \cdot y = y \cdot x$

and 10b -  $x + y = y + x$

$$\text{LHS} = (x_1 \cdot x_3') + (x_1' \cdot x_3)$$

LHS matches RHS of the initial equation

# Practice

**Example 2.4** Consider the logic equation

$$x_1 \cdot \bar{x}_3 + \bar{x}_2 \cdot \bar{x}_3 + x_1 \cdot x_3 + \bar{x}_2 \cdot x_3 = \bar{x}_1 \cdot \bar{x}_2 + x_1 \cdot x_2 + x_1 \cdot \bar{x}_2$$

The left-hand side can be manipulated as follows

$$\begin{aligned}\text{LHS} &= x_1 \cdot \bar{x}_3 + x_1 \cdot x_3 + \bar{x}_2 \cdot \bar{x}_3 + \bar{x}_2 \cdot x_3 && \text{using } 10b \\ &= x_1 \cdot (\bar{x}_3 + x_3) + \bar{x}_2 \cdot (\bar{x}_3 + x_3) && \text{using } 12a \\ &= x_1 \cdot 1 + \bar{x}_2 \cdot 1 && \text{using } 8b \\ &= x_1 + \bar{x}_2 && \text{using } 6a\end{aligned}$$

The right-hand side can be manipulated as

$$\begin{aligned}\text{RHS} &= \bar{x}_1 \cdot \bar{x}_2 + x_1 \cdot (x_2 + \bar{x}_2) && \text{using } 12a \\ &= \bar{x}_1 \cdot \bar{x}_2 + x_1 \cdot 1 && \text{using } 8b \\ &= \bar{x}_1 \cdot \bar{x}_2 + x_1 && \text{using } 6a \\ &= x_1 + \bar{x}_1 \cdot \bar{x}_2 && \text{using } 10b \\ &= x_1 + \bar{x}_2 && \text{using } 16a\end{aligned}$$

16a.  $x + x' \cdot y = x + y$