
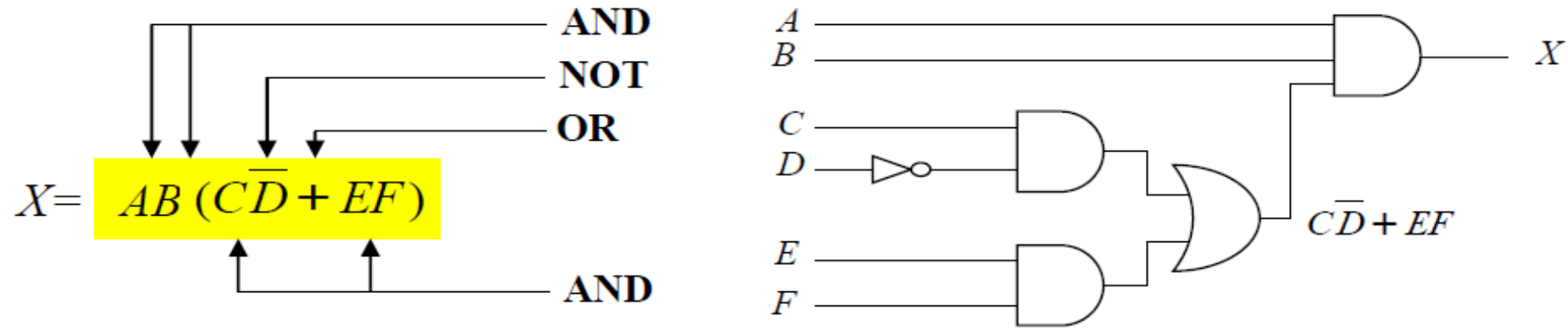


Extra Examples and Exercises DLD

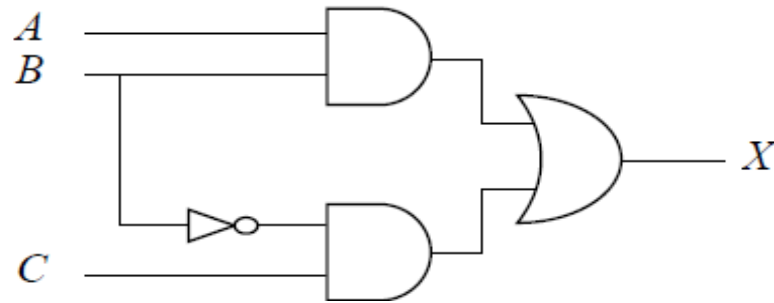Example: Implement the following expression: $X = AB(C\bar{D} + EF)$



Example: Draw the circuit diagram that implements the expression: $X = AB + \bar{B}C$



Example: Prove $(A + B) \cdot (A + C) = A + B \cdot C$

Solution

$$(A + B) \cdot (A + C) = (A + B) \cdot A + (A + B) \cdot C$$

Distributive Law

$$= A \cdot A + B \cdot A + A \cdot C + B \cdot C$$

Distributive Law

$$= A + B \cdot A + A \cdot C + B \cdot C$$

Rule: $A \cdot A = A$

$$= A + A \cdot B + A \cdot C + B \cdot C$$

Commutative Law

$$= A + A \cdot C + B \cdot C$$

Rule: $A + A \cdot B = A$

$$= A + B \cdot C$$

Rule: $A + A \cdot B = A$

Now that you have a taste for the manipulation of Boolean expressions, the next section will show examples of how complex expressions can be simplified.

Example: prove $AB + \bar{A}C + BC = AB + \bar{A}C$

Solution

$$= AB + \bar{A}C + 1 \cdot BC$$

rule $1 \cdot X = X$

$$= AB + \bar{A}C + (A + \bar{A}) \cdot BC$$

rule $X + \bar{X} = 1$

$$= AB + \bar{A}C + ABC + \bar{A}BC$$

Distributive Law

$$= AB + ABC + \bar{A}C + \bar{A}BC$$

Commutative Law

$$= AB(1 + C) + \bar{A}C(1 + B)$$

Distributive Law

$$= AB + \bar{A}C$$


rule $1 + X = 1$

Example: Show $(X + Y) \cdot \bar{X} \cdot \bar{Y} = 0$

$$\begin{aligned}(X + Y) \cdot \bar{X} \cdot \bar{Y} &= (X \cdot \bar{X} \cdot \bar{Y} + Y \cdot \bar{X} \cdot \bar{Y}) \quad (\text{Distributive Law}) \\ &= (X \cdot \bar{X} \cdot \bar{Y} + Y \cdot \bar{Y} \cdot \bar{X}) \quad (\text{Commutative Law}) \\ &= (0 \cdot \bar{Y} + 0 \cdot \bar{X}) \\ &= (0 + 0) \\ &= 0\end{aligned}$$

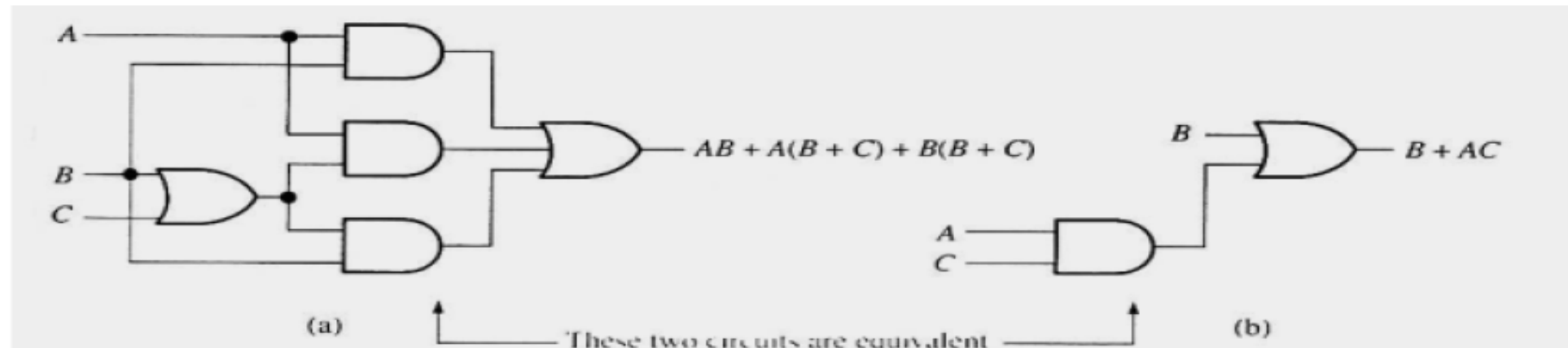Example: determine the truth table and logic diagram $AB + A(B + C) + B(B + C)$

$$\begin{aligned}AB + A(B + C) + B(B + C) &= AB + AB + AC + BB + BC \\ &= AB + AB + AC + B + BC \\ &= AB + AC + B(1 + C) \\ &= AB + B + AC \\ &= B(A + 1) + AC \\ &= B + AC\end{aligned}$$



Example: Prove that $(\overline{X + Y})Z + X\overline{Y} = \overline{Y}(X + Z)$

$$\begin{aligned}
 &= \overline{X} \cdot \overline{Y} \cdot Z + X \cdot \overline{Y} && \text{(DeMorgan's Law)} \\
 &= \overline{Y}(\overline{X} \cdot Z + X) && \text{(Distributive Law)} \\
 &= \overline{Y}(\overline{X} + X)(Z + X) && \text{(Distributive Law)} \\
 &= \overline{Y} \cdot 1(Z + X) && \text{Rule 4} \\
 &= \overline{Y}(Z + X)
 \end{aligned}$$

Example: Simplify the following Boolean Expression $\overline{AB} + \overline{AC} + \overline{ABC}$

Step1: apply DeMoragn's theorem to the first term.

$$(\overline{AB}) \cdot (\overline{AC}) + \overline{ABC}$$

Step2: apply DeMoragn's theorem to each term in parentheses.

$$(\overline{A} + \overline{B})(\overline{A} + \overline{C}) + \overline{ABC}$$

Step3: Apply the distributive law to the two terms in parentheses.

$$\overline{AA} + \overline{AC} + \overline{AB} + \overline{BC} + \overline{ABC}$$

Step4:Apply Boolean Rules $\overline{AA} = \overline{A}$, $\overline{AB} + \overline{ABC} = \overline{AB}(1 + C) = \overline{AB}$

$$\overline{A} + \overline{AC} + \overline{AB} + \overline{BC}$$

Step5: Apply Boolean Rule $\overline{A} + \overline{AC} = \overline{A}(1 + \overline{C}) = \overline{A}$ to the first and second terms

$$\overline{A} + \overline{AB} + \overline{BC}$$

Step6: Apply Boolean Rule $\overline{A} + \overline{AB} = \overline{A}(1 + \overline{B}) = \overline{A}$ to the first and second terms

$$\overline{A} + \overline{BC}$$

Ex Find the 1 – Sum of Minterms 2 – Product of Maxterms of **F**?

1 – Sum of minterms:

$$F = (\bar{X}\bar{Y}Z) + (X\bar{Y}\bar{Z}) + (XYZ) \\ = m_1 + m_4 + m_7 = \sum(1, 4, 7)$$

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

2- Product of Maxterms:

$$F = (X + Y + Z) \cdot (X + \bar{Y} + Z) \cdot (X + \bar{Y} + \bar{Z}) \cdot (\bar{X} + Y + \bar{Z}) \cdot (\bar{X} + \bar{Y} + Z) \\ = M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6 = \prod(0, 2, 3, 5, 6)$$

Ex: Express the function F in Sum of minterms and Product of Maxterms and simplify it

1- Sum of minterms

$$\begin{aligned}
 F(X, Y, Z) &= \bar{X}\bar{Y}\bar{Z} + \bar{X}YZ + X\bar{Y}Z + XY\bar{Z} + XYZ \\
 &= \bar{X}Y(\bar{Z} + Z) + X\bar{Y}Z + XY(\bar{Z} + Z) \\
 &= \bar{X}Y + X\bar{Y}Z + XY = Y(\bar{X} + X) + X\bar{Y}Z = Y + X\bar{Y}Z \\
 &= X\bar{Y}Z + Y = (XZ + Y)(\bar{Y} + Y) = XZ + Y
 \end{aligned}$$

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

H.W.

1. Obtain the canonical product of the sum form of the following function.

$$F(A, B, C) = A + B'C$$

2. Obtain the canonical product of the sum form of the following function.


$$F(A, B, C) = (A + B')(B + C)(A + C')$$

3. Obtain the canonical sum of product form of the following function.

$$F(A, B) = A + B$$

Simplification of Four-Variable Functions

$$F = \sum m(1,3,4,5,10,12,13)$$

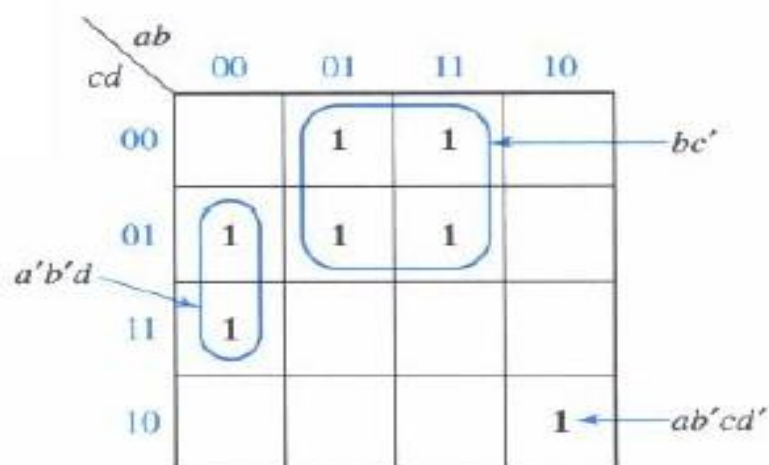

$$F = bc' + a'b'd + ab'cd'$$

DON'T CARE & CAN'T HAPPEN - Examples

Example 1: Simplify the logic function with associated Don't Cares.

$$f(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$$

$$D(w, x, y, z) = \Sigma(0, 2, 5)$$

Don't Care

$$f = \overline{w} \overline{x} + yz$$

		wx					
		00	01	11	10		
y	z	00	X			}	z
		01	1	X			
	11	1	1	1	1		
	10	X					
		x					

DON'T CARE & CAN'T HAPPEN - Examples

Example 2: Simplify the logic function with associated Don't Cares.

$$f(w, x, y, z) = \Sigma(3, 4, 5, 6, 7, 11, 12, 14)$$

$$D(w, x, y, z) = \Sigma(1, 9, 10, 13, 15)$$

Don't Care

$$f = x + z$$

	w				
	x				
	00	01	11	10	
yz	00	1	1		
	01	X	1	X	X
	11	1	1	X	1
	10		1	1	X

Simplification of Incompletely Specified Function

$$F = \sum m(1,3,5,7,9) + \sum d(6,12,13)$$

Karnaugh map for the function $f(a, b, c, d) = a'd + c'd$. The map shows the function's value for all combinations of a, b, c, d . The prime implicants are circled in blue.

$cd \backslash ab$	00	01	11	10
00			X	
01	1	1	X	1
11	1	1		
10		X		

Prime implicants circled in blue:

- $c'd$ (Horizontal group of 4 cells)
- $a'd$ (Vertical group of 4 cells)


$$F = a'd + c'd$$

A POS K-Map

- On a POS K-map, the procedure is the same, except that we map 0's.

	$y+z$	$y+\bar{z}$	$\bar{y}+\bar{z}$	$\bar{y}+z$
$w+x$	0000 0 0	0001 1 1	0011 3 3	0010 2 2
$w+x$	0100 4 4	0101 5 5	0111 7 7	0110 6 6
$\bar{w}+\bar{x}$	1100 C 12	1101 D 13	1111 F 15	1110 E 14
$\bar{w}+x$	1000 8 8	1001 9 9	1011 B 11	1010 A 10


- The simplified expression is: $f = (\bar{w} + \bar{y})$. The simplified circuit is shown at right.

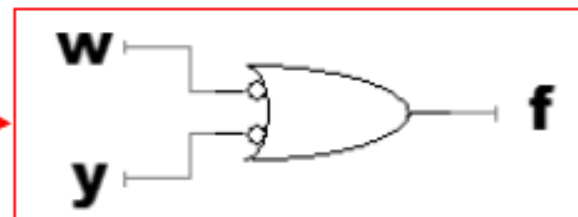

Exercise 4

A truth table and its Boolean expression are shown below, along with the circuit of this unsimplified expression. Use the K-map on the following page to simplify and draw the simplified circuit.

w	x	y	z	f
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	1
1	1	1	0	
1	1	1	1	

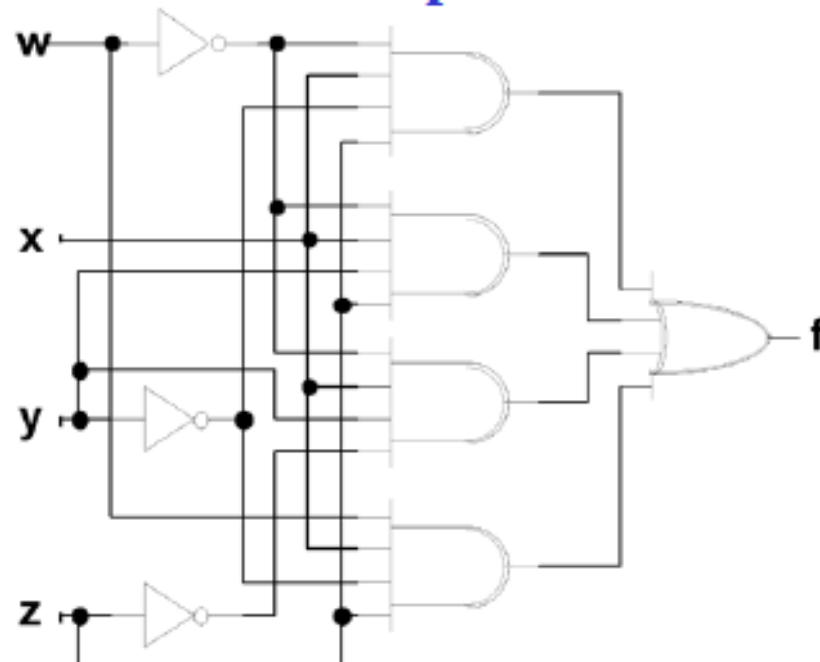

Original Circuit

$$f = \overline{w}x\overline{y}z + \overline{w}xy\overline{z} + w\overline{x}y\overline{z} + w\overline{x}yz$$

Determine the minimum expression for each K-map in figure below:

	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$	1	1	1	1
$\overline{A}B$	1	1	0	0
AB	0	0	0	1
$A\overline{B}$	0	1	1	0

	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$	1	0	1	1
$\overline{A}B$	1	0	0	1
AB	0	0	0	0
$A\overline{B}$	1	0	1	1

Use a K-map to simplify each expression to a minimum SOP form:

(a) $\overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}BC + A\overline{B}\overline{C}$

Ans : No Simplification

(b) $AC[\overline{B} + B(B + \overline{C})]$

Ans : AC

(c) $DEF + \overline{D}\overline{E}\overline{F} + \overline{D}\overline{E}F$

Ans : $\overline{D}\overline{F} + EF$