

# Lecture 4



- SOP
- POS
- K- MAP

AND



A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

74LS08



$$F = AB$$

OR




A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

74LS32



$$F = A + B$$

NOT

 

A	F
0	1
1	0

74LS04



$$F = \overline{A}$$

# Synthesis

## Definitions

- Variable
  - Represents a quantity (0 or 1); typically inputs
- Literal
  - Appearance of a variable (repetition included)
- Product Term
  - Product of literals
- Minterm
  - product term whose literals include **every variable** of the function exactly once in true or complemented form
- Sum-of-Products (SOP) form
  - ORing of product terms;  $abc + abc'$
  - Note:  $(a + b)c$  is not in SOP form

$$F(a,b,c)=a'b'c+ab$$

Variables:  $a, b, c$

Literal:  $a, a', b, b', c$

Product:  $a'b'c, ab$

Minterm:  $a'b'c$



Sum-of-Products:  $a'b'c+ab$

# Synthesis

## Sum-of-Products Form

---

- List of minterms for a 3-variable table
  - Rows numbered to easily identify minterms
  - Notation  $m_i$  denotes minterm for a particular row

Row number	x1	x2	x3	Minterm
0	0	0	0	$m_0 = x_1'x_2'x_3'$
1	0	0	1	$m_1 = x_1'x_2'x_3$
2	0	1	0	$m_2 = x_1'x_2x_3'$
3	0	1	1	$m_3 = x_1'x_2x_3$
4	1	0	0	$m_4 = x_1x_2'x_3'$
5	1	0	1	$m_5 = x_1x_2'x_3$
6	1	1	0	$m_6 = x_1x_2x_3'$
7	1	1	1	$m_7 = x_1x_2x_3$

## Sum-of-Products Form

---

- Canonical sum-of-products form
  - If each product in sum-of-product form is a minterm
- Properties of canonical form
  - Exactly one canonical form
  - Objects that have the same canonical form are the same

## Sum-of-Products Form

- Derive sum-of-product form for the following truth table

Row number	x1	x2	x3	F	Minterm
0	0	0	0	0	$m_0 = x_1'x_2'x_3'$
1	0	0	1	1	$m_1 = x_1'x_2'x_3$
2	0	1	0	0	$m_2 = x_1'x_2x_3'$
3	0	1	1	0	$m_3 = x_1'x_2x_3$
4	1	0	0	1	$m_4 = x_1x_2'x_3'$
5	1	0	1	1	$m_5 = x_1x_2'x_3$
6	1	1	0	1	$m_6 = x_1x_2x_3'$
7	1	1	1	0	$m_7 = x_1x_2x_3$

$F = m_1 \cdot 1 + m_4 \cdot 1 + m_5 \cdot 1 + m_6 \cdot 1$   
 $F = m_1 + m_4 + m_5 + m_6$   
 $F = x_1'x_2'x_3 + x_1x_2'x_3' + x_1x_2'x_3 + x_1x_2x_3'$   
 $F(x_1, x_2, x_3) = \Sigma(m_1, m_4, m_5, m_6)$   
 $F(x_1, x_2, x_3) = \Sigma(1, 4, 5, 6)$

# Maxterm

- Maxterms
  - Complement of minterm
    - $m_0' = M_0$
  - DeMorgan's Theorem –  $(xy)' = x' + y'$
- List of maxterms for 3-input table listed below
  - Notation  $M_i$  denotes maxterm for a particular row

Row number	x1	x2	x3	Minterm	Maxterm
0	0	0	0	$m_0 = x_1'x_2'x_3'$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = x_1'x_2'x_3$	$M_1 = x_1 + x_2 + x_3'$
2	0	1	0	$m_2 = x_1'x_2x_3'$	$M_2 = x_1 + x_2' + x_3$
3	0	1	1	$m_3 = x_1'x_2x_3$	$M_3 = x_1 + x_2' + x_3'$
4	1	0	0	$m_4 = x_1x_2'x_3'$	$M_4 = x_1' + x_2 + x_3$
5	1	0	1	$m_5 = x_1x_2'x_3$	$M_5 = x_1' + x_2 + x_3'$
6	1	1	0	$m_6 = x_1x_2x_3'$	$M_6 = x_1' + x_2' + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = x_1' + x_2' + x_3'$

## Product-of-Sum Form

- Product-of-sum form
  - Function can be represented as maxterms with corresponding value of  $f=0$  ANDed together

Row number	x1	x2	F	Maxterm
0	0	0	1	$M_0 = x1 + x2$
1	0	1	0	$M_1 = x1 + x2'$
2	1	0	0	$M_2 = x1' + x2$
3	1	1	1	$M_3 = x1' + x2'$

$$F = M_1 \cdot M_2$$

$$F = (x1 + x2')(x1' + x2)$$

- More concise form uses row-number subscripts to specify a given function
  - $\Pi$  symbol denotes logical sum

$$F(x1, x2) = \Pi(M_1, M_2)$$

$$F(x1, x2) = \Pi(1, 2)$$

## Product-of-Sum Form

- Derive product-of-sum form for the following truth table

Row number	x1	x2	x3	F	Maxterm
0	0	0	0	0	$M_0 = x1 + x2 + x3$
1	0	0	1	1	$M_1 = x1 + x2 + x3'$
2	0	1	0	0	$M_2 = x1 + x2' + x3$
3	0	1	1	0	$M_3 = x1 + x2' + x3'$
4	1	0	0	1	$M_4 = x1' + x2 + x3$
5	1	0	1	1	$M_5 = x1' + x2 + x3'$
6	1	1	0	1	$M_6 = x1' + x2' + x3$
7	1	1	1	0	$M_7 = x1' + x2' + x3'$

$$F = M_0 \cdot M_2 \cdot M_3 \cdot M_7$$

$$F = (x1 + x2 + x3)(x1 + x2' + x3)(x1 + x2' + x3')(x1' + x2' + x3')$$

$$F(x1, x2, x3) = \prod(M_0, M_2, M_3, M_7)$$

$$F(x1, x2, x3) = \prod(0, 2, 3, 7)$$



## Product-of-Sum Form

Is sum-of-products and product-of-sums really equivalent?

Row number	x1	x2	F	Minterm	Maxterm
0	0	0	0	$m_0 = x1'x2'$	$M_0 = x1 + x2$
1	0	1	0	$m_1 = x1'x2$	$M_1 = x1 + x2'$
2	1	0	1	$m_2 = x1x2'$	$M_2 = x1' + x2$
3	1	1	1	$m_3 = x1x2$	$M_3 = x1' + x2'$

**According to our definitions...**

**Sum-of-products**

$$F = m_2 + m_3$$

$$F = (x1x2') + (x1x2)$$

**Product-of-sums**

$$G = M_0 \cdot M_1$$

$$G = (x1 + x2)(x1 + x2')$$

Complement of a function indicates when output is 0

$$F' = m_0 + m_1$$

$$F' = (x1'x2') + (x1'x2)$$

Complement of  $F'$  should then indicate when output is 1

$$F'' = ((x1'x2') + (x1'x2))'$$

$$F'' = (x1'x2')' (x1'x2)'$$

$$F'' = (x1 + x2)(x1 + x2')$$

Matches

Remember DeMorgan's Theorem


$$15a. (x \cdot y)' = x' + y'$$

$$15b. (x + y)' = x' \cdot y'$$

# NAND and NOR Logic Networks

 
## NAND and NOR Truth Table

- NAND and NOR gate truth tables
- NAND and NOR gates are popular because the underlying implementation is simpler (we'll see in Chapter 3)



**NAND**

a	b	F
0	0	1
0	1	1
1	0	1
1	1	0

 

**NOR**

a	b	F
0	0	1
0	1	0
1	0	0
1	1	0

# NAND and NOR Logic Networks

## DeMorgan Theorem as Logic Circuits

- Can we use NAND and NOR gates to implement various logic circuits?
  - Let's look at logic gate implementation of DeMorgan's Theorem



$$15a. (x_1x_2)' = x_1' + x_2'$$




$$15b. (x_1 + x_2)' = x_1'x_2'$$

Note that the NOT gates are represented as inversion bubbles


# NAND and NOR Logic Networks
 
## DeMorgan Theorem as Logic Circuits


- Any function can be implemented in sum-of-products form
  - We can transform into a network using only NAND gates



general sum-of-products form

 

 connections between AND and OR gates includes 2 INV gates –functionally equivalent  
 $\bar{\bar{x}} = x$



Network can be transformed into a network of NAND gates


Just showed this equivalency – DeMorgan's Theorem




# NAND and NOR Logic Networks
 
## DeMorgan Theorem as Logic Circuits


- Any function can be implemented in product-of-sums form
- We can transform into a network using only NOR gates



general product-of-sums form

 

 
connections between OR and AND gates  
includes 2 INV gates –functionally equivalent  
9.  $x'' = x$




Network can be transformed into a network of  
NOR gates

 Just showed this equivalency – DeMorgan's Theorem







(a) POS implementation

 

(b) NOR implementation

  **Figure 2.29** NOR-gate realization of the function in Example 2.13.

 


**Figure 2.30** NAND-gate realization of the function in Example 2.10.



# Introduction to Optimization and Trade-off

- We now know how to build digital circuits
  - How can we build **better** circuits?
- Let's consider two important design criteria
  - Delay – the time from inputs changing to new correct stable output
    - Every gate has delay of “**1 gate-delay**”
    - Ignore inverters
  - Size – the number of transistors
    - Every circuit has **cost**  
= **number of gates + number of gate inputs**
    - Ignore inverters






Transforming F1 to F2 represents an **optimization**: Better in all criteria of interest


   
# Introduction to Optimization and Trade-off

- Trade-off
  - Improves some, but worsens other, criteria of interest




Transforming G1 to G2 represents a *tradeoff*. Some criteria better, others worse.


# Optimization through Algebraic Manipulation

- Algebraic manipulation

- Multiply out to sum-of-products, then, apply following as much possible
  - $a\mathbf{b} + a\mathbf{b}' = a(\mathbf{b} + \mathbf{b}') = a*1 = a$
  - Combining terms to eliminate a variable
  - (Formally called the “Uniting theorem”)


$$\begin{aligned}F &= xy\mathbf{z} + xy\mathbf{z}' + x'y'\mathbf{z}' + x'y'\mathbf{z} \\F &= xy(\mathbf{z} + \mathbf{z}') + x'y'(\mathbf{z} + \mathbf{z}') \\F &= xy*1 + x'y'*1 \\F &= xy + x'y'\end{aligned}$$

- Duplicating a term sometimes helps
  - Note that doesn't change function
  - $c + d = c + d + d = c + d + d + d + d \dots$


$$\begin{aligned}F &= x'y'z' + \mathbf{x'y'z} + x'yz \\F &= x'y'z' + \mathbf{x'y'z} + \mathbf{x'y'z} + x'yz \\F &= x'y'(z+z') + x'z(y'+y) \\F &= x'y' + x'z\end{aligned}$$

- Algebraic Manipulation

- Which “rules” to use and when?
- Easy to miss “seeing” possible opportunities to combine terms

- K-map contains  $2^n$  cells (or squares) for  $n$  variables.
- Each cell in K-map corresponds to one row of the Truth Table and one minterm of the canonical Boolean function.
- Cells are identified by labelling the edges of the map in such a way as to give a unique combination of variables & their inverses for each cell.

## General K-map Method

---


### General K-map method

1. Convert the function's equation into sum-of-products form (or truth table)
2. Place 1s in the appropriate K-map cells for each term
3. Cover all 1s by drawing the fewest largest circles, with every 1 included at least once; write the corresponding term for each circle
4. OR all the resulting terms to create the minimized function.

## Generalized two Variables K-map

---

### Two Variable K-map

 

(a) Truth table


(b) Karnaugh map

## Two Variables K-map -Example

- Fill in each cell with corresponding value of F
- Draw circles around **adjacent** 1's
  - Groups of 1, 2 or 4
- Circle indicates optimization opportunity
  - We can remove a variable
- To obtain function OR all product terms contained in circles
  - Make sure all 1's are in at least one circle

$x_1$	$x_2$	$f$
0	0	1
0	1	1
1	0	0
1	1	1

Truth table

 

# Generalized Three Variables K-map

## Three Variable K-map

$x_1$	$x_2$	$x_3$	
0	0	0	$m_0$
0	0	1	$m_1$
0	1	0	$m_2$
0	1	1	$m_3$
1	0	0	$m_4$
1	0	1	$m_5$
1	1	0	$m_6$
1	1	1	$m_7$

(a) Truth table

		$x_1 x_2$			
		00	01	11	10
$x_3$	0	$m_0$	$m_2$	$m_6$	$m_4$
	1	$m_1$	$m_3$	$m_7$	$m_5$




(b) Karnaugh map

REMEMBER: K-map graphically place minterms next to each other when they differ by one variable  
m2 cannot be placed next to m4 ( $x_1'x_2x_3'$ ,  $x_1x_2'x_3'$ )

m2 can be placed next to m6 ( $x_1'x_2x_3'$ ,  $x_1x_2x_3'$ )  
m6 can be placed next to m4 ( $x_1x_2x_3'$ ,  $x_1x_2'x_3'$ )
   
## Generalized Three Variables K-map

- Circles can cross left/right sides
  - Remember, edges are adjacent
  - Minterms differ in one variable only
- Circles must have 1, 2, 4, or 8 cells – 3, 5, or 7 not allowed
  - 3/5/7 doesn't correspond to algebraic transformations that combine terms to eliminate a variable
- Circling all the cells is OK
  - Function just equals 1





## Generalized Three Variables K-map

- Two adjacent 1s means one variable can be eliminated
  - Same as in two-variable K-maps
- Four adjacent 1s means two variables can be eliminated
  - Makes intuitive sense – those two variables appear in all combinations, so one must be true
  - Draw one big circle – shorthand for the algebraic transformations above

Diagram 1: K-map with two adjacent 1s circled.

	yz	00	01	11	10
x	0	0	0	0	0
1		0	0	1	1

The 1s in the bottom row at columns 11 and 10 are circled together. A label 'xy' points to the circle.

Diagram 2: K-map with four adjacent 1s circled.

	yz	00	01	11	10
x	0	0	0	0	0
1		1	1	1	1

The entire bottom row (x=1) is circled together. A label 'x' points to the circle.

Draw the biggest circle possible, or you'll have more terms than really needed

Diagram 3: K-map with two separate circles of four adjacent 1s.

	yz	00	01	11	10
x	0	0	0	0	0
1		1	1	1	1


Two circles are drawn around the 1s in the bottom row. The first circle covers the first two columns (00, 01) and is labeled 'xy'. The second circle covers the last two columns (11, 10) and is labeled 'xy'.



## Three Variables K-map – example -1

Let us try an example


Row number	$x_1$	$x_2$	$x_3$	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

 

## Three Variables K-map – Example -2


Let us try another example

Row number	$x_1$	$x_2$	$x_3$	$f$
0	0	0	0	1
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

 



## Generalized four Variables K-map

$x_1$	$x_2$	$x_3$	$x_4$	
0	0	0	0	$m_0$
0	0	0	1	$m_1$
0	0	1	0	$m_2$
0	0	1	1	$m_3$
0	1	0	0	$m_4$
0	1	0	1	$m_5$
0	1	1	0	$m_6$
0	1	1	1	$m_7$
1	0	0	0	$m_8$
1	0	0	1	$m_9$
1	0	1	0	$m_{10}$
1	0	1	1	$m_{11}$
1	1	0	0	$m_{12}$
1	1	0	1	$m_{13}$
1	1	1	0	$m_{14}$
1	1	1	1	$m_{15}$

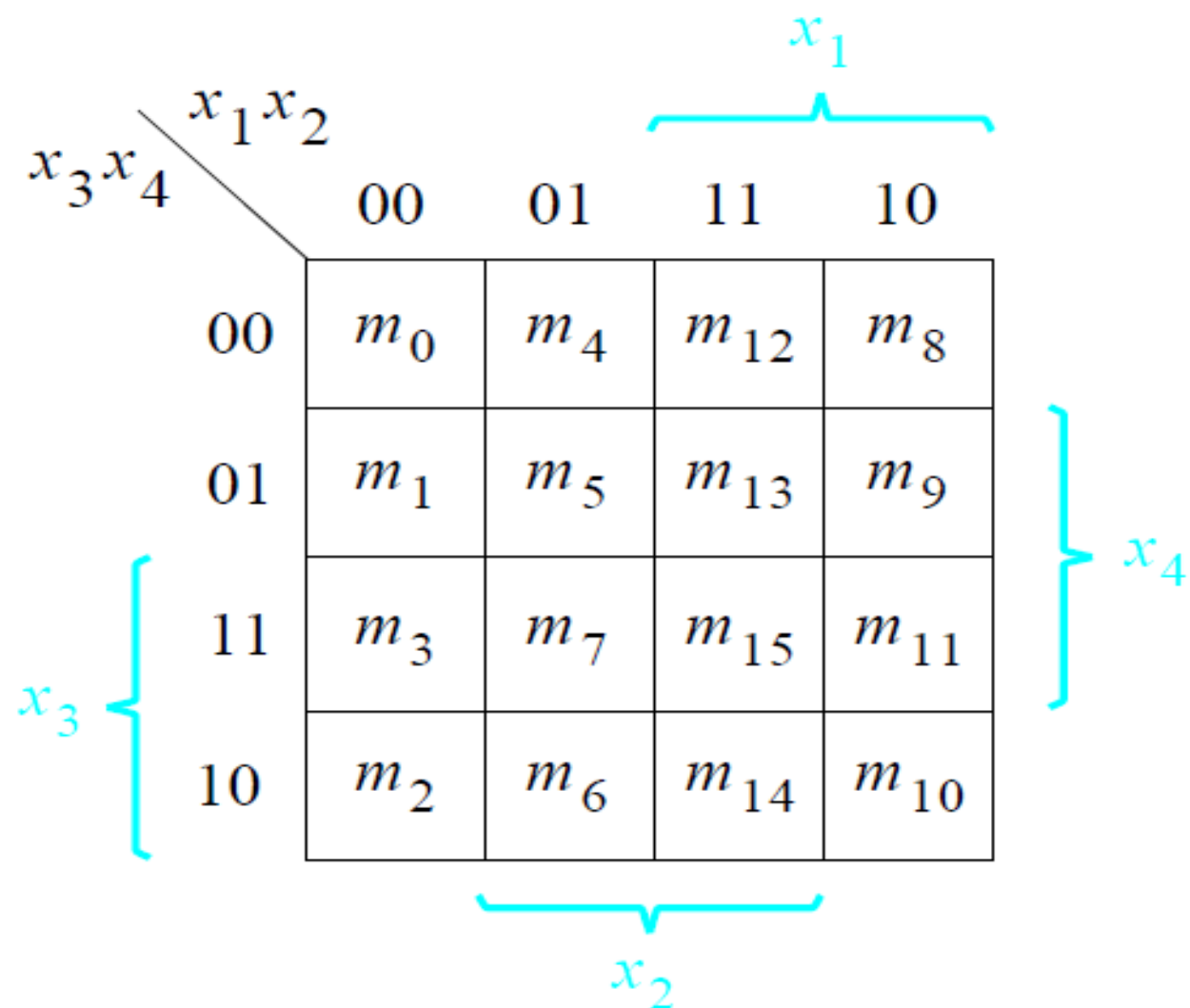

## Generalized Four Variables K-map

- Four-variable K-map follows same principle
  - Left/right adjacent
  - Top/bottom also adjacent
  - Adjacent cells differ in one variable
  - Two adjacent 1's mean one variable can be eliminated
- Four adjacent 1s means two variables can be eliminated
  - Eight adjacent 1s means three variables can be eliminated

  


**Example 1:**  $f(A, B) = \Sigma(0, 1, 2)$


$$F(A, B) = A'B' + A'B + AB'$$

normal way using algebraic manipulation
 
$$\begin{aligned} &= A'(B' + B) + AB' \\ &= A' \cdot 1 + AB' = A' + B' \end{aligned}$$



$$f(A, B) = \bar{A} + \bar{B}$$

 


It is a NAND Gate

Example 2:

$$f(x,y,z) = \Sigma(1,2,6,7)$$

$$f = y\bar{z} + xy + \bar{x}\bar{y}z$$

 

		x			
		00	01	11	10
z	0		1	1	
	1	1		1	


Groupings in the Karnaugh map:

- A group of two cells (1,1) and (1,0) is labeled  $y$ .
- A group of two cells (0,1) and (1,1) is labeled  $x$ .
- A group of two cells (0,0) and (1,0) is labeled  $y$ .

## K-map – Examples – minimize from function

**Example 3:**  $f(x, y, z) = \bar{x}\bar{y} + xy\bar{z} + xyz + x\bar{y}$



$$f = x + \bar{y}$$

 

  **Example 4:**  $f(A, B, C, D) = \Sigma(0, 5, 7, 8, 10, 12, 14)$


$$f(A, B, C, D) = \overline{A}\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}\overline{D} + AB\overline{C}\overline{D} + ABC\overline{D} + \overline{A}B\overline{C}D + \overline{A}BCD + A\overline{B}C\overline{D}$$

$$f = \overline{A}BD + A\overline{D} + \overline{B}\overline{C}\overline{D}$$





# Exercise :

 

DRIVE THE FOLLOWING :

1. Logical function
2. Truth table
3. SOP ,POS minimization
4. K-map minimization

